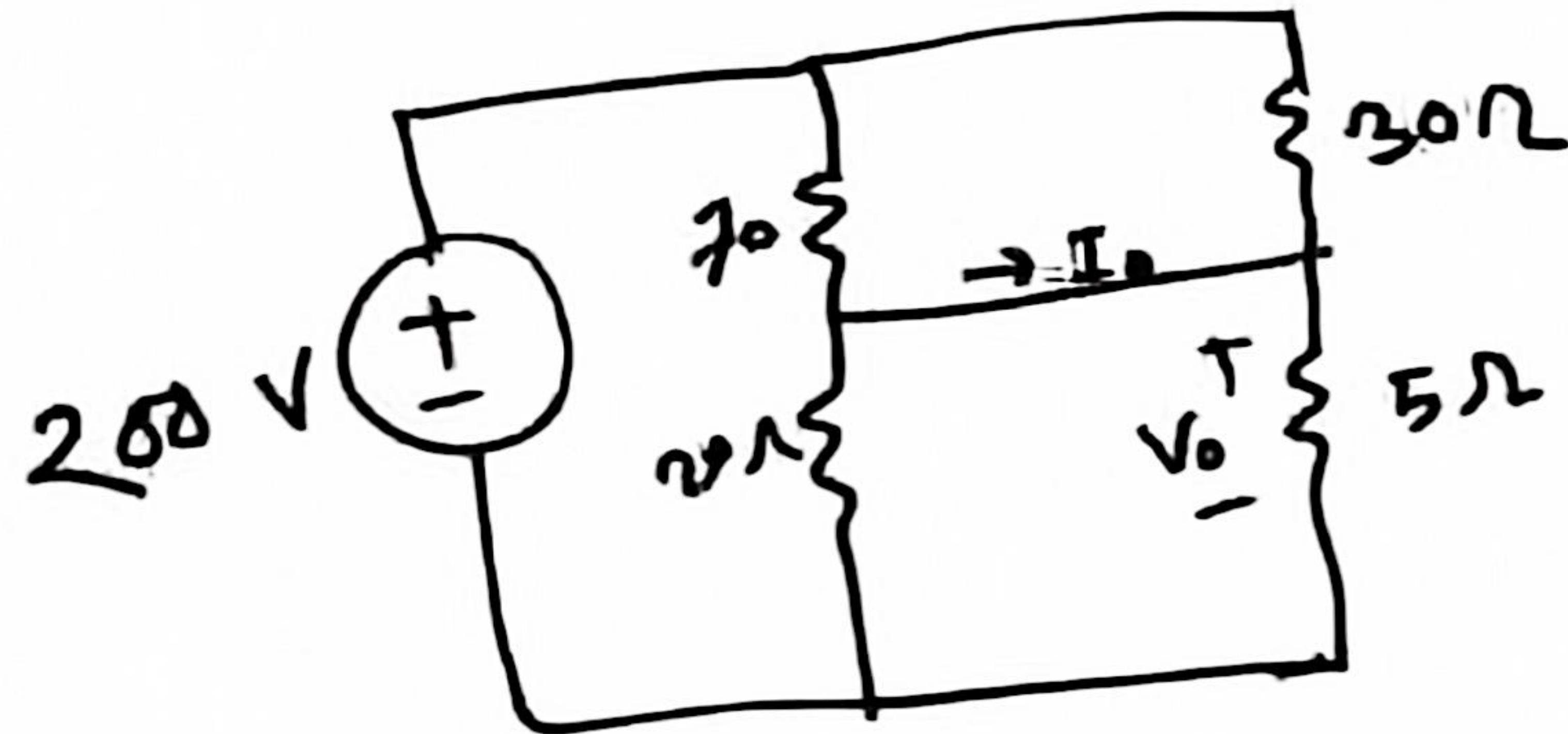


F.M: 20 Time: 20 min

Q.1 calculate V_o by I_o of the following circuit



Q.2. Use node analysis to find V_o of the following circuit

