

University of Dhaka
Affiliated Engineering Colleges
Department of Computer Science and Engineering
1st Year 1st Semester B.Sc. in CSE Final Examination, 2023
EEE-1103: Electrical Circuits

Total Marks: 70

Time: 3 Hours

(Answer any 5 (Five) of the following Questions)

1. a) On which factors the resistance of a material depends? Relate those factors to find the resistance of a material. 3
- b) Why ammeter is connected in series and voltmeter is connected in parallel? Explain. 4
- c) Determine the unknown resistances in Fig. 1.1 given the fact that $R_2 = 5R_1$ and $R_3 = 0.5R_1$ 4
- d) For the network in Fig. 1.2 determine the resistance "R": 3

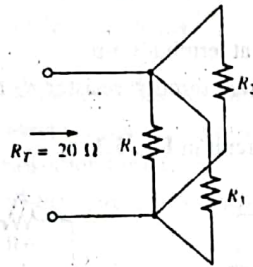


Fig. 1.1

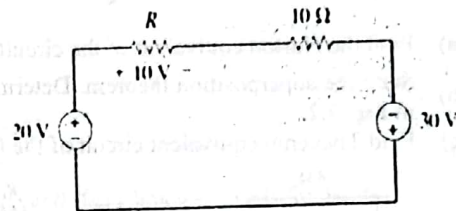


Fig. 1.2

2. a) State Current divider rule with an example. 3
- b) "The total resistance of parallel resistors will always drop as new resistors are added in parallel, irrespective of their value"- explain. 3
- c) Given the information provided in Fig. 2.1, find the unknown quantities: E, R_1 , and I_3 . 4
- d) Determine currents I_4 and I_5 and voltage V_2 in Fig. 2.2. 4

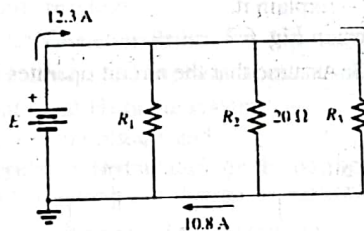


Fig. 2.1

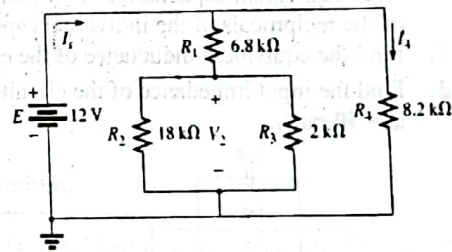


Fig. 2.2

3. a) Explain source conversion technique with an example. 4
- b) What do you mean by open and short circuits? Explain with an example. 3
- c) Find R_{ab} for the circuit in Fig. 3.1. 3
- d) Using a Δ -Y or Y- Δ conversion, find the current I in Fig. 3.2. 4

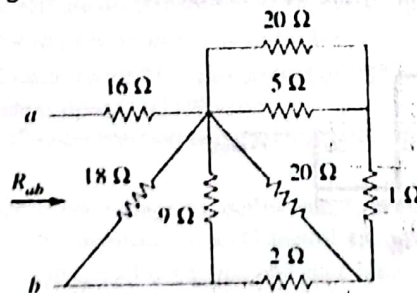


Fig. 3.1

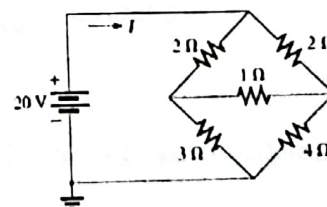


Fig. 3.2

4. a) Write the Mesh Current equations for the circuit in Fig. 4.1. 4
 b) Find the node voltages for the circuit in Fig. 4.2. 4
 c) i. For the network in Fig. 4.3, determine the value of R for maximum power to R . 6
 ii. Determine the maximum power to R .

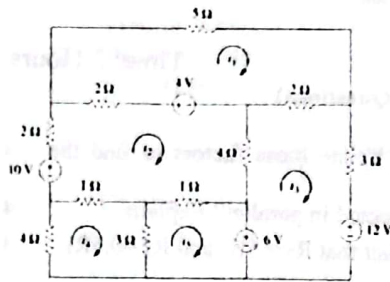


Fig. 4.1

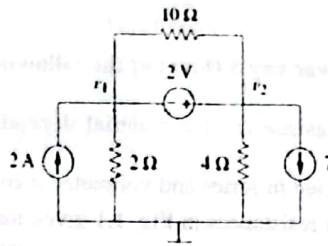


Fig. 4.2

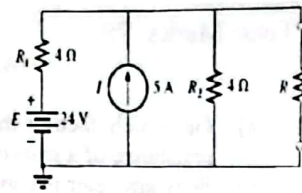


Fig. 4.3

5. a) Find the Norton equivalent of the circuit in Fig. 5.1 at terminals a-b. 4
 b) State the superposition theorem. Determine the current through resistor R_2 for the network in Fig. 5.2. 4
 c) Find Thevenin equivalent circuit of the following circuit in Fig. 5.3. 6

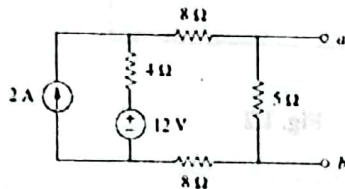


Fig. 5.1

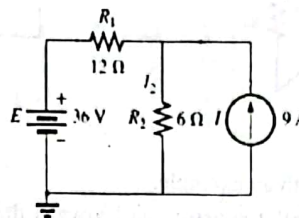


Fig. 5.2

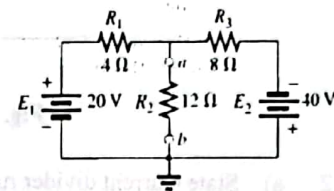


Fig. 5.3

6. a) Obtain the energy stored in each capacitor in Fig. 6.1 under dc conditions. 3
 b) "The equivalent capacitance of 'N' series-connected capacitors is the reciprocal of the sum of the reciprocals of the individual capacitances" – Explain it. 4
 c) Find the equivalent inductance of the circuit shown in Fig. 6.2. 3
 d) Find the input impedance of the circuit in Fig. 6.3. Assume that the circuit operates at $\omega = 50 \text{ rad/s}$. 4

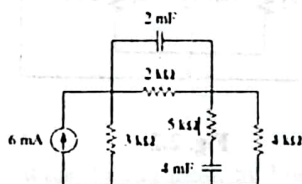


Fig. 6.1

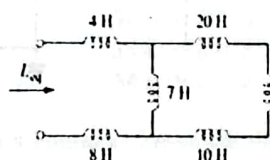


Fig. 6.2

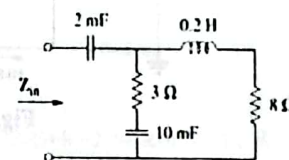


Fig. 6.3

7. a) State and explain Faraday's law of Electromagnetic Induction. 4
 b) Determine the average and rms values of the square wave in Fig. 7.1. 4

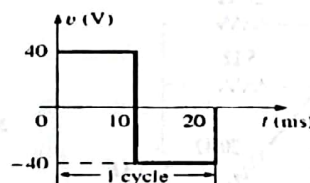


Fig. 7.1

- c) Prove that average power or power dissipated by the ideal inductor is zero watts. 4
 d) What do you mean by admittance and susceptance? 2